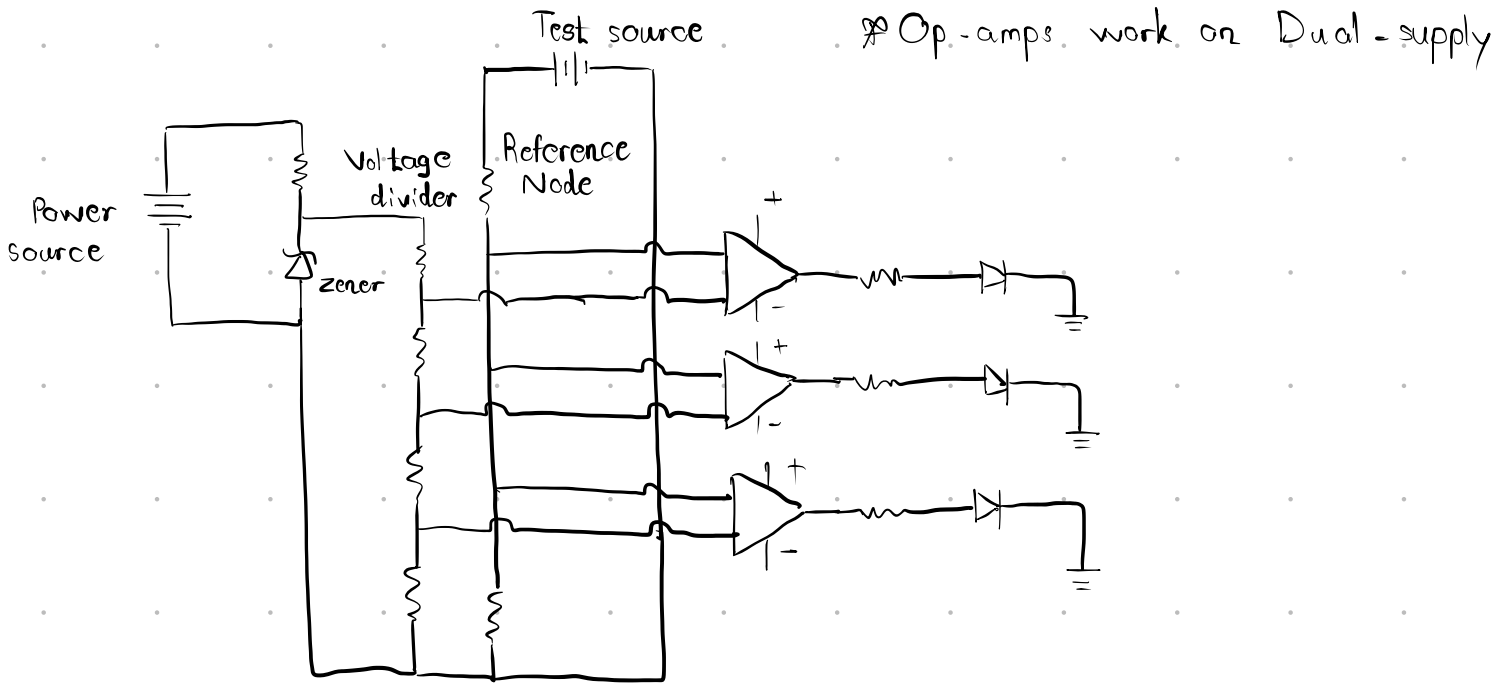


12-V Battery Level Indicator

Calculation



Comparator rule

$$V_+ > V_- \Rightarrow V_{out} = \text{high}$$

$$V_+ < V_- \Rightarrow V_{out} = \text{low}$$

$$V_+ = \text{Non-inverting} \Rightarrow \text{Scaled battery voltage}$$

$$V_- = \text{inverting} \Rightarrow \text{Reference ladder voltage}$$

Why Zener ?

- * Normal diode blocks reverse current.
- * Zener is specially designed for reverse breakdown.
- * When reverse voltage reaches breakdown voltage
 - ① It conducts
 - ② clamps voltage approximately constant

Zener Calculation

$$\text{Supply} = 12\text{V}$$

$$Zener = 5.1V$$

Desired current $\approx 5mA$

$$R = \frac{V_{supply} - V_z}{I}$$

$$R = \frac{12 - 5.1}{0.005}$$

$$R = 1380 \Omega$$

So, $R_z = 1.3k\Omega$ (For assembly)

Why desired current $\Rightarrow 5mA$?

* The current zener needs depends on datasheet values.

Voltage ladder reference $\Rightarrow 5100\Omega$, $V = 5.1V$

$$I = \frac{V}{R} = \frac{5.1}{5100} = 0.001 A = 1mA \checkmark$$

Zener gets $\Rightarrow 4mA \checkmark$ okay

Battery scaling (Test source)

Reference is around only $5.1V$ (because of zener)

$12V$ source needs to be scaled down.

Resistor choice, $R_1 = 1.5k\Omega$

$$R_2 = 1k\Omega$$

$$V = 12 \times \frac{R_2}{R_1 + R_2}$$

$$= 12 \times \frac{1}{1.5 + 1}$$

$$V = 4.8V$$

$$V = 11 \times \frac{R_2}{R_1 + R_2}$$

$$= 11 \times \frac{1}{1.5 + 1}$$

$$= 4.4V$$

12V	Scaled
1V down	0.4V down

So, resistor choice okay $\Rightarrow 1.5k\Omega$ and $1k\Omega$

Reference ladder divider

$$R = \frac{V}{I}$$

$$= \frac{5.1}{0.001}$$

$$R = 5100 \approx 5k\Omega$$

Each voltage step (scaled) from test source is 0.4 V.

LED red $\Rightarrow$ less than 4 V (10V)

LED red + yellow $\Rightarrow$ less than 4.4 V (11V)

LED red + yellow + green $\Rightarrow$ less than 4.8 V (12V)

$$5.1V - 0.3V = 4.8V$$

$$R = \frac{V}{I} = \frac{0.3}{0.001}$$

$$= 300\Omega \approx \text{use } 330\Omega$$

$$V = IR = 0.001 \times 330$$

$$= 0.33V \Leftarrow \text{voltage drop}$$

$$\text{After } R_1 \Rightarrow V = 5.1 - 0.33$$

$$= 4.77 \approx 4.8 \text{ (okay)}$$

$$R_2 = \frac{V}{I} = \frac{0.4}{0.001} = 400 \approx 390\Omega$$

$$R_3 = 390\Omega$$

$$R_4 = 5100 - (330 + 390 + 390)$$

$$= 5100 - (1110)$$

$$= 3990 \approx 3.9k\Omega$$

Resistor choice $\Rightarrow 330 \rightarrow 390 \rightarrow 390 \rightarrow 3900$

Ladder current $\Rightarrow 1\text{mA}$?

It should be larger than op-amp input current.

LM741 $\approx$ around 80nA .

$1\text{mA} \gg 80\text{nA}$ okay $\checkmark$

Why assembly values differ $\Rightarrow 7, 8, 9\text{V}$

Diode we got around 4V or more (Not sure)

Reference ladder $\Rightarrow 4.2\text{V} - 0.3 \Rightarrow 3.9\text{V}$
 $3.9\text{V} - 0.4 \Rightarrow 3.5\text{V}$

Scaled $\Rightarrow 10\text{V} \Rightarrow 4\text{V}$

$\therefore 9\text{V} \Rightarrow 3.6\text{V}$

$9.5\text{V} \Rightarrow 3.8\text{V}$

$9.75\text{V} \Rightarrow 3.9\text{V}$

Threshold for Green became around $9.75 - 10$

Threshold for yellow became around 8.75 which is 3.5 scaled.

Threshold for red became around 7.75 .

In practice our leds light up at around $7, 8, 9$.

So, the circuit concept is correct.

Note: Values can differ according to hardware.